

**KIBABII UNIVERSITY COLLEGE**

*(A Constituent College of Masinde Muliro University of Science Technology)*

P.O. Box 1699-50200 Bungoma, Kenya

Tel. 020-2028660/0708-085934/0734-831729

E-mail: [enquiries@kibabiiuniversity.ac.ke](mailto:enquiries@kibabiiuniversity.ac.ke)

**UNIVERSITY REGULARY EXAMINATIONS****2<sup>ND</sup> SEMESTER 2012 /2013 ACADEMIC YEAR****FOR THE DEGREE OF****BACHELOR OF SCIENCE (COMPUTER SCIENCE)****COURSE CODE: CSC 220****COURSE TITLE: ELECTRONICS****DATE:** 26th August, 2013**TIME:** 9.00a.m – Noon

---

**INSTRUCTIONS TO CANDIDATES:**

Answer Question One and any other two questions from the following Five Questions

**QUESTION ONE (30 MARKS)**

- (a) Distinguish the following as applied to Electronics
- (i) Semiconductors and Insulator
  - (ii) Conduction Band and Valence band
  - (iii) BJT and FET
  - (iv) Donor and acceptor
  - (v) Extrinsic and Intrinsic Semiconductor (10 marks)
- (b) Explain the formation of P type and N-type semiconductors (6 marks)
- (c) With aid of diagrams explain the transistor action (5 marks)
- (d) Show that gain of amplifier with feedback =  $A_i/(1+\beta A_i)$  (5 marks)
- (e) Derive the DC load line equation for transistor amplifier (4 marks)

**QUESTION TWO (20 MARKS)**

- (a) With aid of circuit diagram explain the function of component of Transistor amplifier
- (b) Draw a two stage common emitter circuit (5 marks)
- (c) Draw the h-parameter equivalent circuit for two stage (5 marks)

**QUESTION THREE (20 MARKS)**

- (a) Define the h-Parameter for any two port network. Hence or otherwise determine
- (b) Current Amplification
- (c) Voltage amplification
- (d) Power amplification

**QUESTION FOUR (20MARKS)**

For each of the following amplifier classification determine their maximum efficiency

- (a) Class A (6 marks)
- (b) Class B (6 marks)
- (c) Class C (7 marks)

**QUESTION FIVE (20 MARKS)**

With aid of diagrams explain the principle of operation of the following types of diodes

- (a) PN diode (4 marks)
- (b) Zener diode (6 marks)
- (c) Thyristor (10 marks)